

# **EE463 Hardware Project Simulation Report**

4 December, 2019

Team “Blue Smoke”

Paul Brown – 2463461

İbrahim Duru – 2166304

Mustafa Şahin

## Table of Contents

Formula Sheet.....	3
Introduction.....	4
Simulations.....	4
Voltage Source Model.....	4
Motor Calculations and Modeling.....	4
Three-Phase Thyristor Rectifier Simulation.....	10
Three-Phase Diode Rectifier + Buck Converter Simulation.....	12
TRIAC AC Chopper + Diode Bridge Rectifier.....	14
Topology Comparison and Selection.....	20
Three-Phase Thyristor Rectifier.....	20
Rectifier + Buck Converter.....	20
Single-Phase Thyristor Rectifier.....	20
Chosen Topology: Single-Phase Diac-Controlled Triac rectifier.....	20
Component Selection.....	22
Triac Selection.....	22
Diac Selection.....	22
Capacitor Selection.....	23
Resistor Selection.....	23
Additional Components.....	23
Conclusions.....	23

## Formula Sheet

$$V_t = E_a + I_a \times R_a \quad (1)$$

$$E_a = L_{af} \times I_f \times \omega_m \quad (2)$$

$$T = L_{af} \times I_f \times I_a \quad (3)$$

$$E_a = V_t - I_a \times R_a \quad (4)$$

$$E_a \times \frac{I_a}{\omega_m} = T \quad (5)$$

$$T = P/\omega_m \quad (6)$$

# Introduction

This report presents the designing a rectifier circuit that will be used to operate a DC motor in three possible alternatives ways such that single or three phase thyristor rectifier or diode rectifier with buck convertor.

## Simulations

Simulations were performed for various topologies under consideration to better understand the advantages and disadvantages among them and to show some of the component ratings that would be needed for those topologies to be applied. The topologies simulated were a three-phase thyristor rectifier, a three-phase diode rectifier with buck converter, and a TRIAC-based AC chopper to diode bridge rectifier. The simulation models and results will be shown in following subsections, however, some common assumptions and calculations will be shown first.

### Voltage Source Model

The converter designed in this project will be fed from a variable transformer (variac) adjusted to give the desired output voltage. It is assumed that the variac output voltage will be adjusted to a desired setpoint prior to connecting load to the output of our converter. For the three-phase rectifier and buck converter models, a variac output voltage of  $120 V_{\text{rms,l-n}}$  was selected. This voltage level allows the converters to be in the middle of their regulating range while providing  $175 V_{\text{DC}}$  output.

For the triac-based model, since it is fed from single-phase voltage source and because the diac circuit needs a substantial voltage headroom over the motor back EMF in order to charge, the variac is simulated as set to  $220 V_{\text{rms,l-n}}$ . Based on simulations, this voltage allows the circuit to achieve  $175 V_{\text{DC}}$  (average) output to the motor.

The source impedance of the lab AC power supply and variac is not known, but for modeling purposes, it was represented with a resistance of  $50 \text{ m}\Omega$  and an inductance of  $180 \text{ }\mu\text{H}$ . This works out to an available short-circuit current at  $120 \text{ V}$  of  $1590 \text{ A}$ .

### Motor Calculations and Modeling

In this project, the DC motor load to be driven by the electronic power converter should be represented in the simulations. In Simulink, it is possible to represent the DC motor load as a motor with a torque load or using the  $E_a$ ,  $R_a$ ,  $L_a$  equivalent circuit elements. Both representations were developed for our Simulink model, but for the simulation results, the  $E_a$ ,  $R_a$ ,  $L_a$  equivalent circuit elements were used.

The parameters for the DC motor model were calculated based on the nameplate data of the motor and parameters provided with the project assignment.

The nameplate is shown in Figure 1 below.



*Figure 1: DC Motor Nameplate*

Additional motor parameters were provided with the project assignment. The motor data taken from this information is summarized in Table 1.

*Table 1: DC Motor Provided Parameters*

Parameter	Value
Pmec	5.5 HP
RPM	1500
VS	220 V
IS	23.4 A
Armature Winding	0.8 $\Omega$ , 12.5 mH
Shunt Winding	210 $\Omega$ , 23 H
Interpoles Winding	0.27 $\Omega$ , 12 mH

The DC motor model in Simulink takes some additional parameters that were not provided, but which can be calculated from the available information.

$$\text{Rated speed (rad/s)} = \frac{1500 \times 2 \times \pi}{60} = 157 \text{ rad/s}$$

$$\text{Rated field current (A)} = \frac{220 \text{ V}}{208 \Omega} = 1.06 \text{ A}$$

Simulink also takes parameters for armature-field mutual inductance  $L_{af}$  as well as a friction coefficient. These can be calculated from the provided values for motor

operation at rated speed, power, voltage, and current, as is shown in the following subsection.

### Motor Operation at Rated Load

The equivalent circuit parameters for a DC motor are the following:

$$V_t = E_a + I_a \times R_a \quad (1)$$

$$E_a = L_{af} \times I_f \times \omega_m \quad (2)$$

$$T = L_{af} \times I_f \times I_a \quad (3)$$

(In many formulations,  $K_a \Phi$  is used instead of  $L_{af} I_f$ , but since Simulink will use  $L_{af}$ , it is convenient that we use this formulation.)

$P_{rated} = (5.5 \text{ HP}) \times (746 \frac{W}{HP}) = 4103 \text{ W}$ . This power is mechanical output.

At rated speed of 157 rad/s, rated mechanical torque is  $(4103 \text{ W}) / (157 \text{ rad/s}) = 26.12 \text{ N-m}$ .

Since the motor is rated for a shunt configuration,

$$I_f = \frac{220 \text{ V}}{210 \Omega} = 1.05 \text{ A}$$

Rated electrical input is  $(220 \text{ V}) \times (23.4 \text{ A}) = 5148 \text{ W}$  (neglecting any reactive power). So rated efficiency is approximately 0.80.

Resistive losses in armature =  $(22.4 \text{ A})^2 \times (0.8 \Omega) = 401 \text{ W}$ . Remaining losses are in the field resistance and friction.

At full load  $V_t = 220 \text{ V}$  and  $E_a = V_t - I_a \times R_a = 220 \text{ V} - (0.8 \Omega)(22.4 \text{ A}) = 202 \text{ V}$ . (4)

$$L_{af} = \frac{E_a}{I_f \cdot \omega_m} = \frac{202}{1.05 \times 157} = 1.23 \text{ H}$$

$$L_{af} I_f = 1.05 \text{ A} \times 1.23 \text{ H} = 1.29$$

The electrical torque can be calculated as

$$E_a \times \frac{I_a}{\omega_m} = \frac{(202 \text{ V}) \times (22.4 \text{ A})}{157} = 28.76 \text{ N-m}. \quad (5)$$

Since the rated output mechanical torque is 26.1 N-m, apparently there are additional mechanical torque losses. The simplest is to model them as Coulomb friction losses (i.e. constant torque):

$$T_e - T = 28.76 \text{ N-m} - 26.12 \text{ N-m} = 2.64 \text{ N-m}$$

At rated speed, this works out to friction loss of  
 $2.64 \text{ N-m} \cdot 157 \text{ rad/s} = 415 \text{ W}$ .

### Simulink Parameters

When modeled as a DC motor in Simulink, the parameters entered are as shown in Figure 2.

Armature resistance and inductance [Ra (ohms) La (H) ]	[ 0.8 0.0125]
Field resistance and inductance [Rf (ohms) Lf (H) ]	[ 210 23]
Field-armature mutual inductance Laf (H) :	1.23
Total inertia J (kg.m <sup>2</sup> )	1
Viscous friction coefficient Bm (N.m.s)	0
Coulomb friction torque Tf (N.m)	2.64
Initial speed (rad/s) :	157
Initial field current:	1.05

*Figure 2: DC Motor Simulink Parameters*

When modeled using  $E_a$ ,  $R_a$ , and  $L_a$ ,  $R_a$  and  $L_a$  are entered directly as shown in the datasheet, but back EMF  $E_a$  should be calculated based on the operating speed.  $E_a$  was calculated for rated load above, and is calculated for other load conditions in the following subsections, the results of which are summarized in Table 1. A terminal voltage of 175 V is chosen since the problem specifies that  $V_{\max} < 180 \text{ V}$ , but lower voltages require higher current to get the same power output.

*Table 2: Equivalent  $E_a$  for Various Load Conditions*

Load Condition	$V_t$ (V)	$E_a$ (V)	$\omega_m$ (rad/s)	External T (N-m)
Starting	175	0	0	283
No Load	175	171	133	2.6
Kettle Load (1600 W)	175	164	127	15.4
Rated Load	220	202	157	26.1

### Startup

At startup,  $\omega_m = 0$ , so  $E_a = 0$ .

Torque and current at startup will depend on how much voltage is applied. If full rated voltage were applied, startup current would be

$$I_a = \frac{175 \text{ V}}{0.8 \Omega} = 219 \text{ A}$$

$$T = 219 \times 1.29 = 283 \text{ N-m}$$

This is too much current and torque, so the applied voltage must be reduced for starting the motor.

### No Load

The motor running at no load has only to output mechanical power equal to the friction of the running motor and coupled AC synchronous machine.

Neglecting voltage drop on the armature winding such that  $E_a = V_t$ , speed can be estimated as

$$\frac{E_a}{L_{af} \cdot \omega_m} = \frac{175}{1.29} = 136 \text{ rad/s}$$

Based on the coefficient of friction calculated in the full load section above, the mechanical power at this speed can be estimated as  
 $2.65 \text{ N-m} \times 136 \text{ rad/s} = 360 \text{ W}$

Estimating additionally that the connected synchronous machine has a similar amount of friction, the total "no load" load is estimated as 700 W.

At no-load, this friction loss will have the following circuit values:

$$V_t = 175 \text{ V}$$

$$I_a \times E_a = 700 \text{ W} \Rightarrow E_a = \frac{700 \text{ W}}{I_a}$$

$$\frac{700 \text{ W}}{I_a} = 175 \text{ V} - I_a \times (0.8 \Omega)$$

$$700 \text{ W} = (175 \text{ V}) \times I_a - I_a^2 \times (0.8 \Omega)$$

$$0 = 0.8 \times I_a^2 - 175 \times I_a + 700$$

$$I_a = \frac{175 - \sqrt{175^2 - 4 \times 0.8 \times 700}}{2 \times 0.8} = 4.1 \text{ A.}$$

$$E_a = \frac{700 \text{ W}}{4.1 \text{ A}} = 171 \text{ V}$$

No-load speed can be calculated as

$$\omega_m = \frac{E_a}{L_{af} \cdot I_f} = \frac{171 \text{ V}}{1.29} = 133 \text{ rad/s.}$$



This is  $133/157 = 85\%$  of rated speed.

The external torque to account for the synchronous generator friction is estimated as  
 $350 \text{ W} / 133 \text{ rad/s} = 2.6 \text{ N-m}$

### Kettle Load

For the “Robust Design” bonus, the motor must be run such that it supplies power to a 1600-W water kettle connected to the output of the synchronous machine coupled to the DC motor. Based on the additional friction load calculated for “no-load” operation, the total mechanical power for the kettle load is 2300 W.

The kettle load is calculated to have the following circuit values:

$$V_t = 175 \text{ V}$$

$$I_a \times E_a = 2300 \text{ W} \Rightarrow E_a = \frac{2300 \text{ W}}{I_a}$$

$$\frac{2300 \text{ W}}{I_a} = 175 \text{ V} - I_a \times (0.8 \Omega)$$

$$2300 \text{ W} = (175 \text{ V}) \times I_a - I_a^2 \times (0.8 \Omega)$$

$$0 = 0.8 \times I_a^2 - 175 \times I_a + 2300$$

$$I_a = \frac{175 - \sqrt{175^2 - 4 \times 0.8 \times 2300}}{2 \times 0.8} = 14.0 \text{ A.}$$

$$E_a = \frac{2300 \text{ W}}{14.0 \text{ A}} = 164 \text{ V}$$

Speed can be calculated as

$$\omega_m = \frac{E_a}{L_{af} \cdot I_f} = \frac{164 \text{ V}}{1.29} = 127 \text{ rad/s.}$$

This is  $\frac{127}{157} = 81\%$  of rated speed.

At  $\omega_m = 127 \text{ rad/s}$ , the estimated 1950 W external mechanical load will have a torque of

$$T = P/\omega_m = \frac{1950}{127} = 15.4 \text{ N-m.} \quad (6)$$

## Three-Phase Thyristor Rectifier Simulation

The three-phase thyristor rectifier was simulated in Simulink using the built-in thyristor blocks. The firing signal was provided by the power toolbox pulse generator. Since in some cases the load current is discontinuous, the double firing option had to be selected in the pulse generator in order to ensure that each thyristor was able to conduct through both pulses in its sequence.

In each load scenario, the firing angle  $\alpha$  was adjusted to give an average output voltage of 175 V for the no-load and kettle load scenarios and 220 V for the full load scenario. For the load scenario of motor starting, a firing angle close to  $90^\circ$  was selected such that the motor current was around rated current or less.

Thyristors were modeled with typical data rather than as ideal switches. Thyristors were modeled with a forward voltage drop of 1.5 V and on-state resistance of  $0.001 \Omega$ .

Although there were several load scenarios simulated, a single Simulink model was created, and the parameters were adjusted by a script for each load condition. The common model for the three-phase thyristor rectifier simulations is shown in Figure 3.

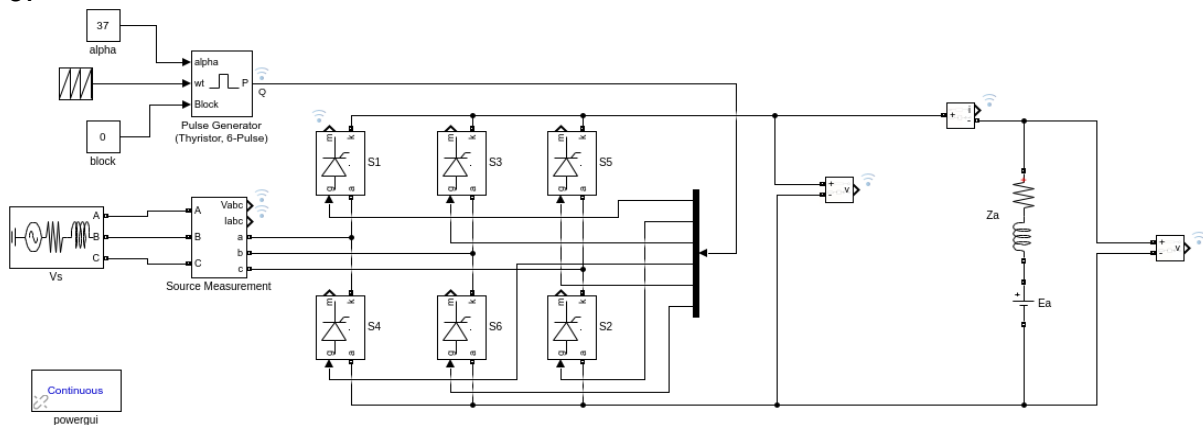


Figure 3: Three-Phase Thyristor Rectifier Simulink Model

Summary values of the simulation results are shown in Table 3 and Table 4.

Table 3: Three-Phase Thyristor Rectifier Simulation Summary (Input Side)

Load	$\alpha$	$V_{IN}$ (V <sub>RMS</sub> )	$I_{IN}$ (A <sub>RMS</sub> )	$P_{IN}$ (W)	$Q_{IN}$ (var)	$S_{IN}$ (VA)	PF	$I_{IN}$ THD (%)
Starting	87	119.6	9.99	62.43	1193	1194	0.05	37.2
No Load	53	119.8	3.79	242.6	383.2	453.6	0.53	59.71
Kettle Load	50	119.3	11.39	823.2	1082	1360	0.61	33.02
Rated Load	36	118.9	18.53	1688	1416	2203	0.77	30.72

*Table 4: Three-Phase Thyristor Rectifier Simulation Summary (Output Side)*

<b>Load</b>	<b>V<sub>OUT</sub> (V<sub>AVG</sub>)</b>	<b>V<sub>OUT</sub> Ripple</b>	<b>I<sub>OUT</sub> (A<sub>AVG</sub>)</b>	<b>I<sub>OUT</sub> Ripple</b>	<b>P<sub>OUT</sub> (W)</b>	<b>Efficiency (%)</b>
Starting	10.16	284.9	11.89	10.41	124.4	66.45
No Load	174.3	207.9	4.08	6.62	715	98.23
Kettle Load	175.5	218.5	13.72	8.27	2414	97.73
Rated Load	220.8	167.6	22.54	6.84	4978	98.31

Table 5 shows some key values that would be needed to select/size the thyristors for this circuit if more detailed design were to be carried out. Note that the power is conduction loss in each thyristor based on the typical forward voltage drop of 1.5 V and  $R_{on}$  of 1 m $\Omega$  that was used. If this topology were selected, for a more accurate simulation, the simulation could be repeated with parameters of the selected thyristor devices.

*Table 5: Thyristor Key Values*

<b>Load</b>	<b>I<sub>avg</sub> (A)</b>	<b>I<sub>RMS</sub> (A)</b>	<b>V<sub>max</sub> Rev.</b>	<b>V<sub>max</sub> Fwd.</b>	<b>P<sub>loss</sub> (W)</b>
Starting	3.98	7.09	290.1	293.3	6.02
No Load	1.36	2.68	292.6	221.3	2.05
Kettle Load	4.56	8.00	292.1	225.4	6.9
Rated Load	7.48	12.98	292.5	173.8	11.38

The output voltage and current waveforms for the various load scenarios are shown in Figure 4.

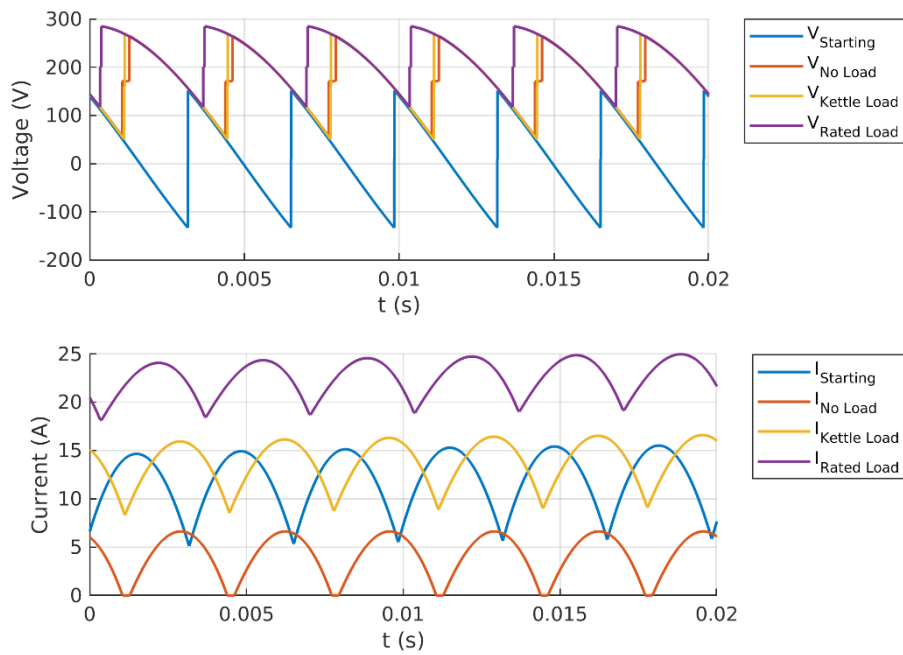


Figure 4: Three-Phase Thyristor Rectifier Simulated Waveforms

### Three-Phase Diode Rectifier + Buck Converter Simulation

The second circuit type that was simulated was a three-phase diode rectifier with buck converter on the DC side. The converter was modeled with a switching speed of 10 kHz. A DC-side filter capacitor of 1000  $\mu\text{F}$  was included. The buck converter L was selected as 0.1 mH and C was selected as 100  $\mu\text{F}$ . These values were chosen to give reasonably good ripple on the DC bus and the output. If this topology were selected, these values would require further investigation and refinement.

Diodes were modeled with typical voltage drop of 0.8 V while the MOSFET was modeled with typical on-state resistance of 0.1  $\Omega$ . Equivalent series resistance was neglected for capacitors and the inductor in the circuit.

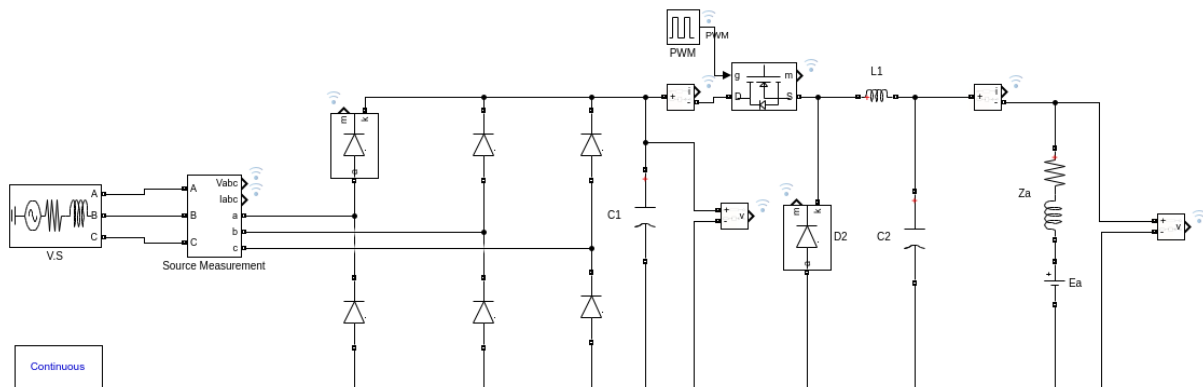


Figure 5: Buck Converter Simulink Model

For each load condition, the MOSFET duty cycle was adjusted to give an average output voltage appropriate to the load condition. For the motor start, this was set to a small duty cycle to obtain current near or less than the rated current of the motor. For no load and kettle load conditions, the output voltage was adjusted to 175 V, and for the rated load case, the output voltage was adjusted to 220 V.

Summary values of the simulation results are shown in Tables 6, 7, and 8.

*Table 6: Buck Converter Simulation Summary (Input Side)*

<b>Load</b>	<b>D</b>	<b>V<sub>IN</sub> (V<sub>RMS</sub>)</b>	<b>I<sub>IN</sub> (A<sub>RMS</sub>)</b>	<b>P<sub>IN</sub> (W)</b>	<b>Q<sub>IN</sub> (var)</b>	<b>S<sub>IN</sub> (VA)</b>	<b>PF</b>	<b>I<sub>IN</sub> THD (%)</b>
Starting	4	120	0.88	51.25	91.86	105.2	0.49	178.4
No Load	25	119.9	4.7	339.8	449.6	563.6	0.6	130.8
Kettle Load	41	119.6	11.14	887.1	994.5	1333	0.67	110.2
Rated Load	75	119.3	19.78	1673	1664	2360	0.71	96.94

*Table 7: Buck Converter Simulation Summary (DC Bus)*


<b>Load</b>	<b>V<sub>D</sub> (V<sub>AVG</sub>)</b>	<b>V<sub>D</sub> Ripple</b>	<b>I<sub>D,OUT</sub> (A<sub>AVG</sub>)</b>	<b>I<sub>D,OUT</sub> Ripple</b>	<b>P<sub>D,OUT</sub> (W)</b>
Starting	290.5	1.32	0.53	19.68	153
No Load	288.2	7.07	3.52	28.87	1013
Kettle Load	285.9	15.73	9.25	47.58	2645
Rated Load	283.3	24.51	17.59	51.91	4991

*Table 8: Buck Converter Simulation Summary (Output Side)*

<b>Load</b>	<b>V<sub>OUT</sub> (V<sub>AVG</sub>)</b>	<b>V<sub>OUT</sub> Ripple</b>	<b>I<sub>OUT</sub> (A<sub>AVG</sub>)</b>	<b>I<sub>OUT</sub> Ripple</b>	<b>P<sub>OUT</sub> (W)</b>	<b>Efficiency (%)</b>
Starting	10.79	2.31	13.17	0.41	142.1	92.43
No Load	175.6	3.18	5.72	0.08	1005	98.57
Kettle Load	175.9	10.12	14.86	0.29	2613	98.18
Rated Load	219.9	21.35	22.42	0.78	4932	98.24

If we were designing the buck converter in detail, the key simulation values for each component could be examined, but as there are several components in the model and the purpose of these simulations was general comparison of the topologies, the detailed tabulation of component voltages & currents is not presented in this report.

The output voltage and current waveforms for the various load scenarios are shown in Figure 6.

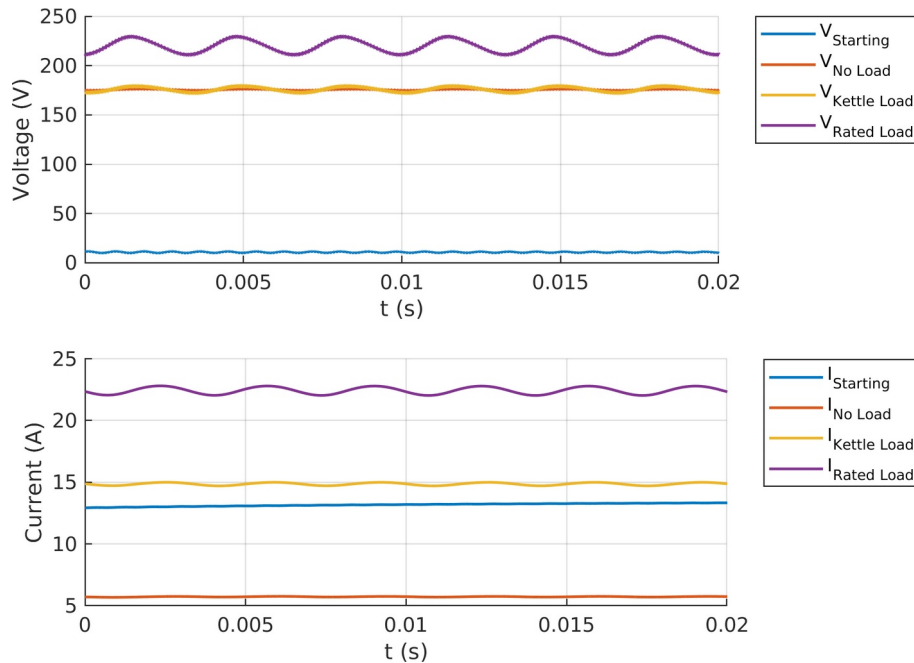


*Figure 6: Buck Converter Simulated Waveforms*

In Figure 6, we can see how the ripple on the DC bus shows up in the output voltage even though the MOSFET is switching at a much higher speed. This is because the model is using a fixed duty cycle, without any feedback or feedforward to regulate the output voltage. With an adaptive duty cycle control, the output voltage could be regulated much closer to a desired setpoint even though the intermediate DC bus has significant ripple, especially at high load currents.

## **TRIAC AC Chopper + Diode Bridge Rectifier**

The last topology that was considered is a simple triac AC chopper circuit connected to the DC motor through a diode bridge. This topology was not presented in class, but when asked about how to generate the gate signals for a thyristor rectifier, he suggested that we could use triac and diac components and recommended basic driver circuits. After some research on possible thyristor driver circuits, we found a circuit in the Littlefuse “Phase Control Using Thyristors” Application Note AN1003 that we thought could possibly work for this project. The circuit as shown in the application note is reproduced in Figure 7.

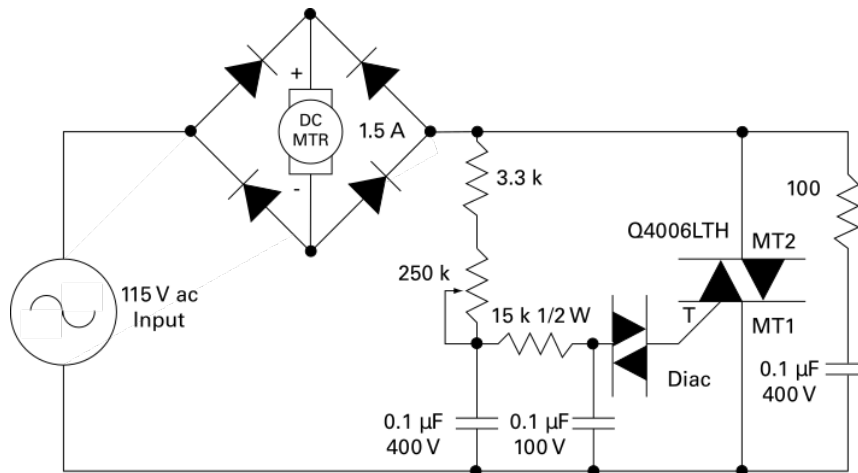

*Figure 7: TRIAC DC Motor Control Circuit*


Simulating this circuit is complicated in Simulink by the fact that Simulink does not have any triac or diac models in the toolbox. In order to implement the circuit in Simulink, a triac model was developed by placing two thyristors in parallel but with opposite polarity and connecting the firing signals together. The input resistance of the triac gate was modeled with a resistance of 1 k $\Omega$  since that gives a gate current pulse of 10-20 mA when the diac fires and seems to be in the right order of magnitude.

A Simulink diac model was created by making the same counter-parallel connection as was done for the triac and then creating logic in the firing circuit such that the diac fires when the voltage across the device exceeds its characteristic turn-on voltage. For the purposes of preliminary simulations, a diac breakover voltage  $V_{bo}$  of 36 V was used since this appears to be a commercially available rating.

Figure 8 shows the full triac-based Simulink model.





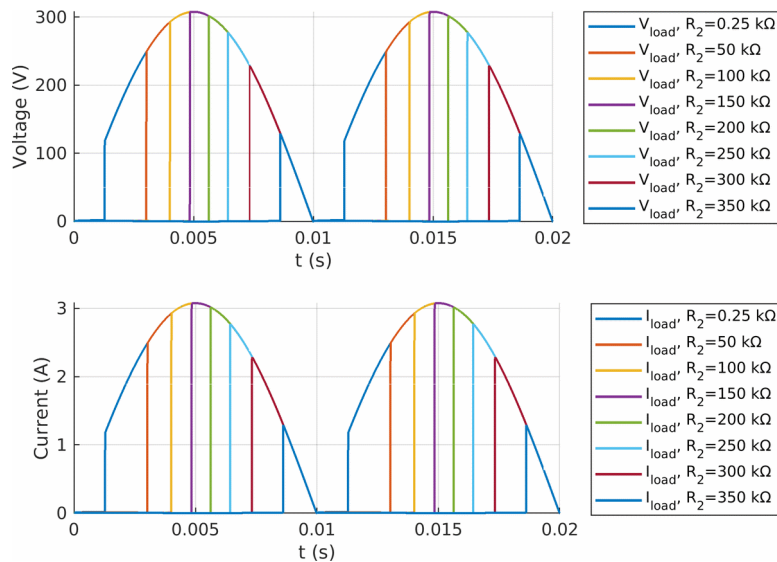

*Figure 9: Triac-Diac Simulink Results with Small Resistive Load*

As can be seen from Figure 9, the diac firing circuit is limited in its ability to fire at angles near  $0^\circ$  and near  $90^\circ$ . We think that this is probably owing to the inclusion of series resistor  $R_1$  that prevents the capacitors from being short-circuited if the potentiometer is adjusted to its minimum position.

### DC Motor Load

Once the circuit was simulated using the small resistive load and was giving reasonable results, we passed to simulations using the equivalent circuit for the DC motor as we did for the other topologies. For each load condition, the  $R_2$  resistance was adjusted to give an average output voltage appropriate to the load condition. For the motor start, this was set to obtain current near or less than the rated current of the motor. For no load and kettle load conditions, the output voltage was adjusted to 175 V. In this case, the rated motor load was not simulated since a phase-to-neutral supply voltage of 220 V was not sufficient to obtain an output voltage of  $220 V_{DC}$ . Since the problem statement restricts the output voltage to less than  $180 V_{DC}$  anyway, the rated load simulation is not essential to the project.

Figure 10 shows the output voltage and current waveforms for the simulations of the triac-based control model.

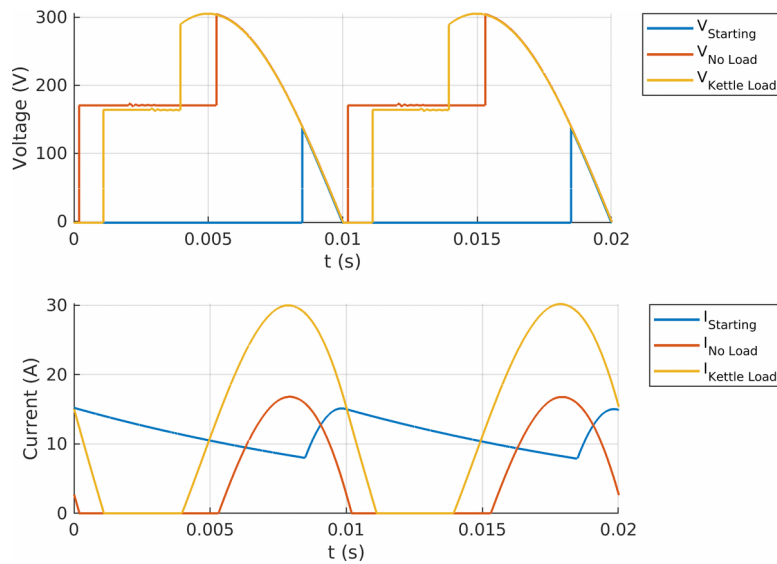


Figure 10: Triac-Diac Simulation Output Waveforms

In Figure 10, we can see that the output current is continuous only for the starting case. In the other two load cases, current was discontinuous. This is largely due to the use of a single-phase AC voltage source rather than three-phase.

Tables 9 and 10 show summary values of the input and output side voltages and currents from the simulations.

Table 9: Triac-Diac Simulation Summary (Input Side)

Load	R2 (k $\Omega$ )	V <sub>IN</sub> (V <sub>RMS</sub> )	I <sub>IN</sub> (A <sub>RMS</sub> )	P <sub>IN</sub> (W)	Q <sub>IN</sub> (var)	S <sub>IN</sub> (VA)	PF	I <sub>IN</sub> THD (%)
Starting	190	219.8	7.07	199.3	1541	1554	0.13	133.5
No Load	25	219.5	7.68	878.1	1439	1686	0.52	66.62
Kettle Load	20	218.8	17.64	2505	2936	3859	0.65	40.31

Table 10: Triac-Diac Simulation Summary (Output Side)

Load	V <sub>OUT</sub> (V <sub>AVG</sub> )	V <sub>OUT</sub> Ripple	I <sub>OUT</sub> (A <sub>AVG</sub> )	I <sub>OUT</sub> Ripple	P <sub>OUT</sub> (W)	Efficiency (%)
Starting	11.47	153.4	14.46	8.69	170.9	85.76
No Load	174.8	304.8	4.77	15.56	863	98.27
Kettle Load	175	307.1	13.45	30.2	2463	98.33

Since this topology ended up being selected, additional key information about components was extracted from the simulations and is shown in Tables 11, 12, 13, and 14. These values are used for preliminary component selection.

Table 11: Triac-Diac Simulation Key Diode Values

Load	$I_{avg}$ (A)	$I_{RMS}$ (A)	$V_{MAX}$ (V)	$P_{Loss}$ (W)
Starting	7.23	8.16	152.6	5.85
No Load	2.39	5.43	304	1.94
Kettle Load	6.7	12.49	306.3	5.52

Table 12: Triac-Diac Simulation Key Triac Values

Load	$I_{avg}$ (A)	$I_{RMS}$ (A)	$V_{MAX}$ (V)	$P_{Loss}$ (W)
Starting	3.04	7.07	311.1	4.61
No Load	4.77	7.68	138.6	7.21
Kettle Load	12.84	17.64	128.8	19.57

Table 13: Triac-Diac Simulation Key Capacitor Values

Load	$C_1 I_{RMS}$ (A)	$C_1 V_{MAX}$ (V)	$C_2 I_{RMS}$ (A)	$C_2 V_{MAX}$ (V)
Starting	0.95	42.67	2.39	36
No Load	1.64	59.79	2.38	36
Kettle Load	1.64	56.68	2.38	36

Table 14: Triac-Diac Simulation Key Resistor Value

Load	$R_1 I_{RMS}$ (mA)	$R_1 P$ (mW)	$R_2 I_{RMS}$ (mA)	$R_2 P$ (mW)	$R_3 I_{RMS}$ (mA)	$R_3 P$ (mW)
Starting	1.04	1.08	1.04	205.3	0.82	10.05
No Load	1.77	3.12	1.77	78.09	1.03	15.82
Kettle Load	1.73	3	1.73	60.06	0.94	13.35

# Topology Comparison and Selection

Each of the topologies considered will be discussed briefly.

## Three-Phase Thyristor Rectifier

This circuit offers us higher output average voltage and less ripple compared to the other alternatives without using parallel output capacitor. However, it requires six thyristors and required gate signal driver circuits. As we can see from the table 3, in order to arrange the feedback and behavior of circuit, we need to change the firing angle of thyristor. In addition, number of thyristor is more than our chosen topology. This effects the size and cost of the project. As a result, in order to work toward compactness and simplicity bonuses, this topology was judged as not appropriate.

## Rectifier + Buck Converter

This circuit offers us a simpler way to finish the project compared to the three-phase thyristor rectifier. However, it requires six diodes and a buck convertor part. In addition, arranging the filter and the calibration of buck convertor without using a microcontroller can be problem. Similar to our opinion for the three-phase thyristor rectifier, in order to work toward compactness and simplicity bonuses, this topology was judged as not appropriate.

## Single-Phase Thyristor Rectifier

This circuit offers us more simple way compared to the three-phase thyristor rectifier. However, it has less output voltage and more ripple comparing to a three-phase rectifier. Again, in this topology, we need to drive four thyristors in synchronism with each other. In addition to that, according feedback data from the output firing angle of the four thyristors should be changed. The gains in eliminating two thyristors to drive still did not achieve the level of simplicity that we desired.

## Chosen Topology: Single-Phase Diac-Controlled Triac rectifier

The single-phase diac-controlled triac rectifier has several advantages for which we selected it. The primary advantage is its simplicity. There is a single controlled element, the triac, for which a gate signal is required. The diac can be used to control the triac by adjusting the value of the variable resistor in the circuit. Because the control circuit is powered from the mains voltage, no additional power supply or regulation is needed for the control circuit as it would be in other configurations.

One disadvantage of this topology is that it is not easily adapted to any type of feedback control. It is also limited to single-quadrant operation by the diode bridge that supplies the DC motor load.

If we are successful in implementing a working circuit using the diac for controlling the triac, we could explore other, more flexible methods for control that would allow feedback control, especially to limit current during motor start-up.

*Table 15: Comparison According to Components*

<b>Topology</b>	<b>Required Semiconductor</b>	<b>Required Manageable Components</b>
3-phase Thyristor	6 Thyristor	6 Thyristor
Rectifier+ Buck	6 Diode + Mosfet	Mosfet
1- phase Thyristor	4 Thyristor	4 Thyristor
Diac- Triac	4 Diode+ 1 Diac+ 1 Triac	1 Diac

*Table 16: Comparison According to Bonuses*

<b>Topology</b>	<b>Industrial Design Bonus</b>	<b>Robust Design Bonus</b>	<b>Closed-loop Voltage/Current Control Bonus</b>
3-phase Thyristor	Applicable	Applicable	Need to change in firing angle
Rectifier+ Buck	Applicable	Applicable	Need to change in mosfet signal
1- phase Thyristor	Applicable	Applicable	Need to change in firing angle
Diac- Triac	Applicable	Applicable	Need to change in resistance value

*Table 17: Comparison According to Bonuses (continued)*

<b>Topology</b>	<b>Compactness Bonus</b>	<b>Simplicity Bonus</b>	<b>Four-Quadrant Bonus</b>
3-phase Thyristor	Too much component	Can be hard due to firing	Applicable
Rectifier+ Buck	Too much component	Can be hard due to mosfet signal	Not Applicable
1- phase Thyristor	Applicable	Can be hard due to firing	Not Applicable
Diac- Triac	Applicable with ease	Easy thanks to diac- triac	Not Applicable

Final words about the choosing the topology;

We need to decide what bonuses we want to aim. In order to be in the safe side, simplicity bonus is chosen. Complexity of the topologies are due to controlling thyristor or MOSFET. Thanks to diac-triac, we are dealing this complexity easily. Also, compactness bonus is achievable with this topology thanks to simplicity of the circuit. As a result, topology is chosen according to which bonuses we can achieve and what cost.

## Component Selection

### Triac Selection

In all possible cases, we observe 311 V<sub>max</sub>. Current value depends on how we start to system. Therefore, we choose a tentative value for the current. In order to be safe side we choose BTA26-600 Triac.

Symbol	Parameter	BTA24 <sup>(1)</sup>	BTB24	BTA25 <sup>(1)</sup>	BTA26 <sup>(1)</sup>	BTB26	T25	Unit
I <sub>T(RMS)</sub>	RMS on-state current	25	25	25	25	25	25	A
V <sub>DRM</sub> /V <sub>RRM</sub>	Repetitive peak off-state voltage	600 / 800	600 / 800	600 / 800	600 <sup>(2)</sup> / 800	600	600 / 800	V
I <sub>GT</sub> (Snubberless)	Triggering gate current	35 / 50	35 / 50	50	35 / 50	-	35	mA
I <sub>GT</sub> (Standard)	Triggering gate current	-	50	50	50	50	-	mA

Figure 11: Triac Ratings

### Diac Selection

First we checked the Digikey for the possible components. However, most of the components were obsolete. Then, we look the Direnc.net, we find DB3 DO-35 36 V DIAC. It is appropriate for the circuit since its blocking voltage is similar to our expected voltage. In addition, in the circuit diac does not carry too much current so 2A current rating is useful for the circuit.

Symbol	Parameter		Value		Units
			DB3	DB3TG	
V <sub>BO</sub>	Break-over Voltage @ C=22nF	Min.	28	30	V
		Typ.	32	32	V
		Max.	36	34	V
±V <sub>BO</sub>	Break-over Voltage Symmetry @ C=22nF	Max.	±3	±2	V
I <sub>BO</sub>	Break-over Current @ C=22nF	Max.	100	15	μA
Δ V	Dynamic Break-over Voltage @ I <sub>BO</sub> to I <sub>F</sub> =10mA	Min.	5	9	V
I <sub>B</sub>	Leakage Current @ V <sub>B</sub> =0.5V <sub>BO</sub> (Max.)	Max.	10		μA
V <sub>O</sub>	Output Voltage *see diagram 1	Min.	5		V
P <sub>D</sub>	Power Dissipation		150		mW
I <sub>FRM</sub>	Repetitive Peak Forward Current, Pulse Width=20μsec		2		A

Figure 12: Diac Ratings

## Capacitor Selection

In our reference circuit, capacitor value is given as 0.1uf 400 V. We did some changes in reference circuit and we are still in range of capacitor so we can use that values for capacitor. According to this values we choose Ceramic disc capacitor.

*Figure 13: Capacitor Ratings*

QUICK REFERENCE DATA	
DESCRIPTION	VALUE
Ceramic Class	2
Ceramic Dielectric	Y5V
Voltage (V <sub>AC</sub> )	400
Min. Capacitance (pF)	9000
Max. Capacitance (pF)	100 000
Mounting	Radial

## Resistor Selection

We have not specified resistance values. According to starting method, desired performance we are changing our resistance values. While choosing the resistance values, we should be careful about the current that passing through the resistor and power rating of the resistor.

## Additional Components

In addition to these main components, we need a circuit board, heatsinks for the semiconductors, maybe a cooling unit. Moreover, we would like to add a feedback unit. According to feedback, we need additional materials.

## Conclusions

In this report, we have described our groups' efforts to examine several controlled rectifier topologies, simulation results for the topologies considered, and compared the advantages and disadvantages of various options. We selected a diac-controlled triac topology and examined the necessary ratings based on simulations, selecting the major components needed for the circuit.

We look forward to the valuable feedback that we will receive from the course instructor & assistant for this project. While we have made an effort to simulate the circuit as best we could, we look forward to getting into the lab with the components, testing a prototype, and working out any issues that may appear.