



# Blue Smoke Team Hardware Project


Paul Brown  
İbrahim Duru  
Mustafa Şahin

11 December 2019

## Topology Options

1. Three-phase thyristor rectifier (SCR)
2. Three-phase diode rectifier + buck converter
3. Single-phase thyristor rectifier (SCR)
4. Single-Phase Diac-Controlled Triac Rectifier

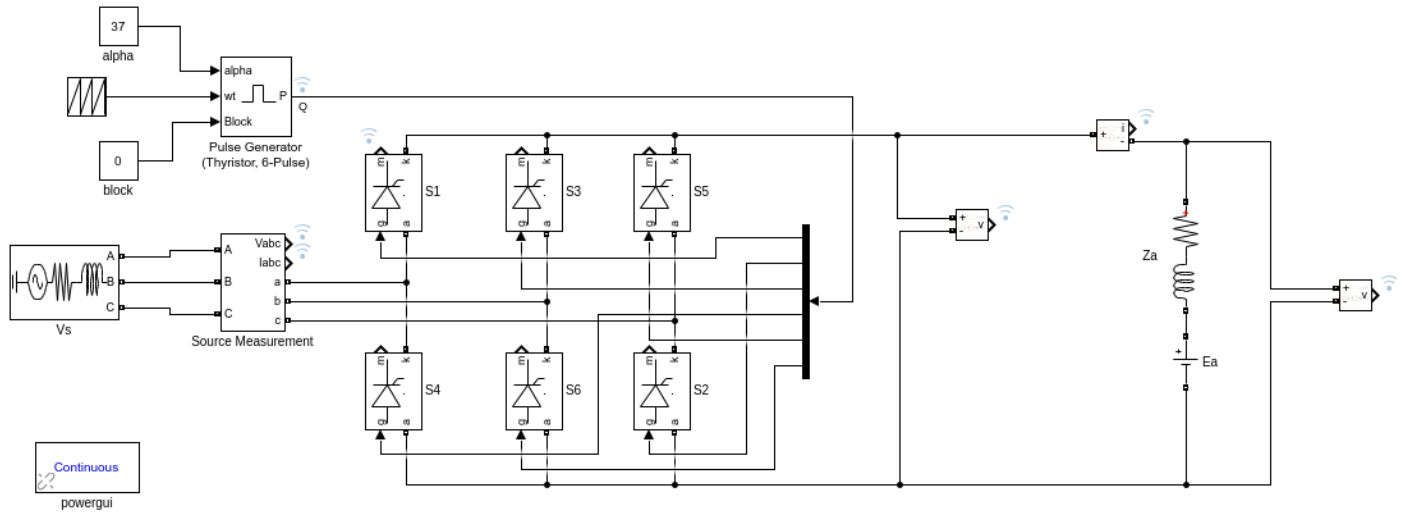
## Option 1: Three-phase Thyristor Rectifier (SCR)



## Option 1: Three-phase Thyristor Rectifier (SCR)

Advantages	Disadvantages
<ul style="list-style-type: none"><li>• Higher average output voltage attainable</li><li>• Less ripple compared to single-phase rectifier</li></ul>	<ul style="list-style-type: none"><li>• Requires firing circuits for six thyristors</li><li>• Firing control must be synchronized with input AC voltage</li></ul>

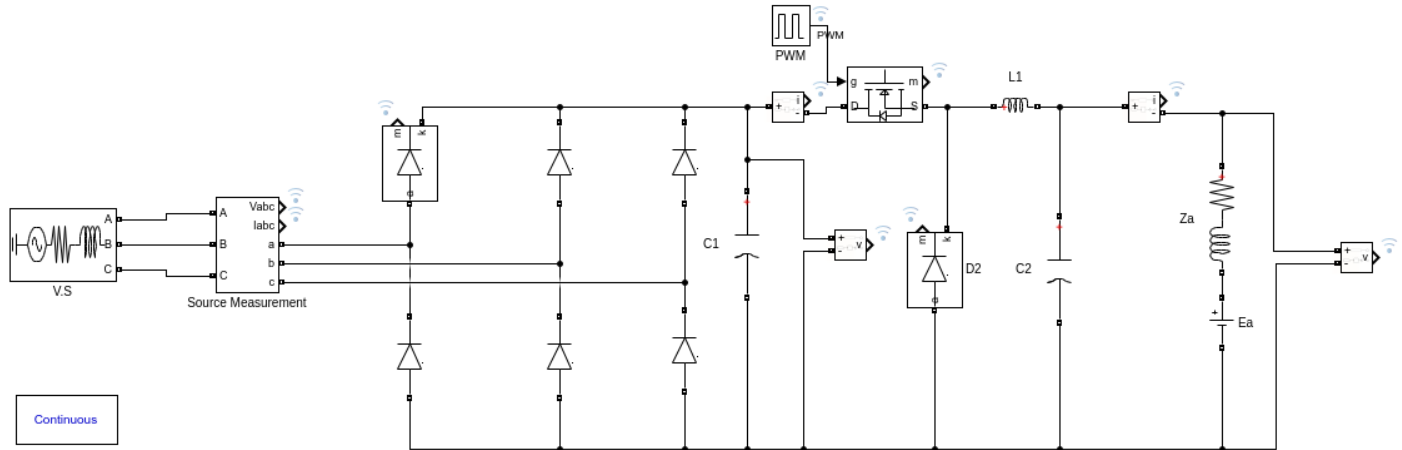
## Option 2: Diode Rectifier + Buck Converter



## Option 2: Diode Rectifier + Buck Converter

Advantages	Disadvantages
<ul style="list-style-type: none"><li>• Fast and accurate control of output is possible</li></ul>	<ul style="list-style-type: none"><li>• Requires capacitor &amp; inductor</li><li>• Many components</li></ul>
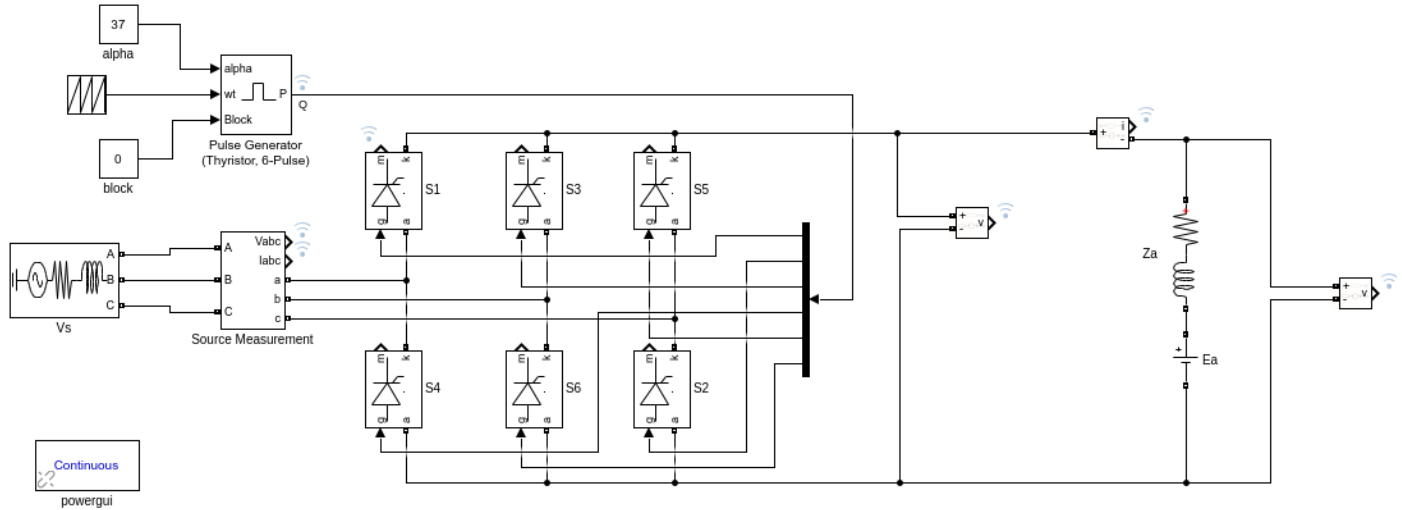
## Option 3: Single-phase Thyristor Rectifier (SCR)



## Option 3: Single-phase Thyristor Rectifier (SCR)

Advantages	Disadvantages
<ul style="list-style-type: none"><li>• Fewer thyristors compared to three-phase (4 vs 6)</li></ul>	<ul style="list-style-type: none"><li>• Available output voltage is less compared to three-phase AC input</li><li>• Still requires firing circuits for four thyristors</li><li>• Firing control must be synchronized with input AC voltage</li></ul>



## Single-Phase Diac-Controlled Triac Rectifier


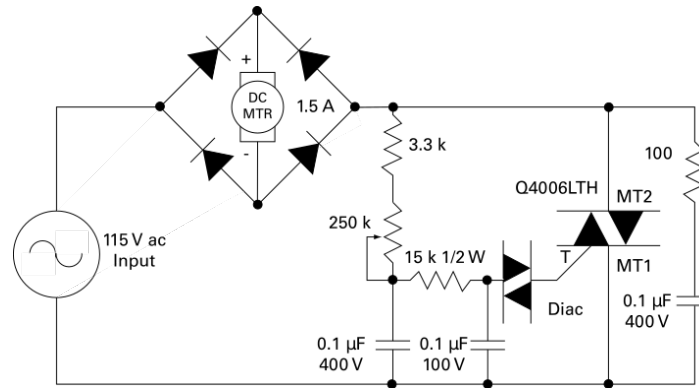


Figure 1. Circuit Diagram from Littlefuse Application Note AN1003

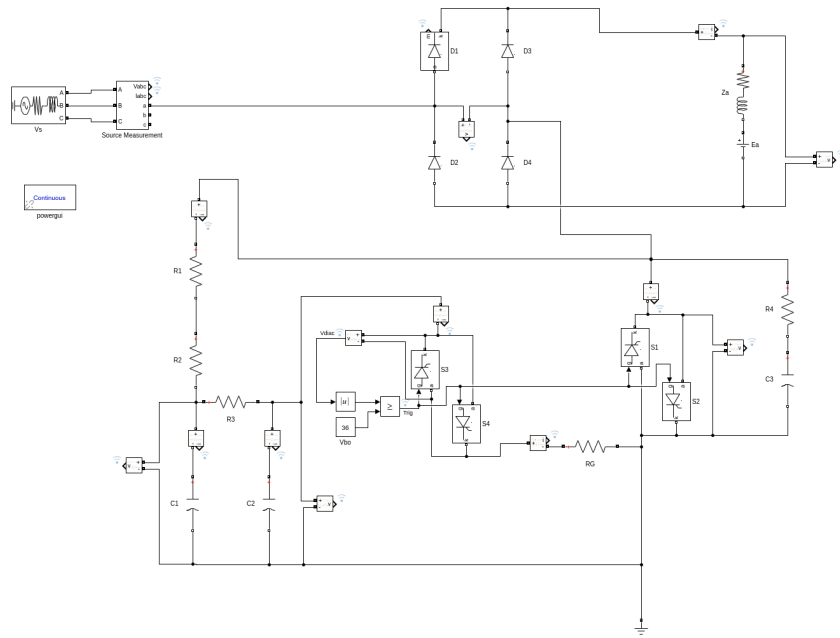
# Single-Phase Diac-Controlled Triac Rectifier




## Single-Phase Diac-Controlled Triac Rectifier

Advantages	Disadvantages
<ul style="list-style-type: none"><li>• Circuit is very simple with few components</li><li>• Single control circuit needed</li></ul>	<ul style="list-style-type: none"><li>• Introduction of feedback control difficult to incorporate</li></ul>

# Simulation Results

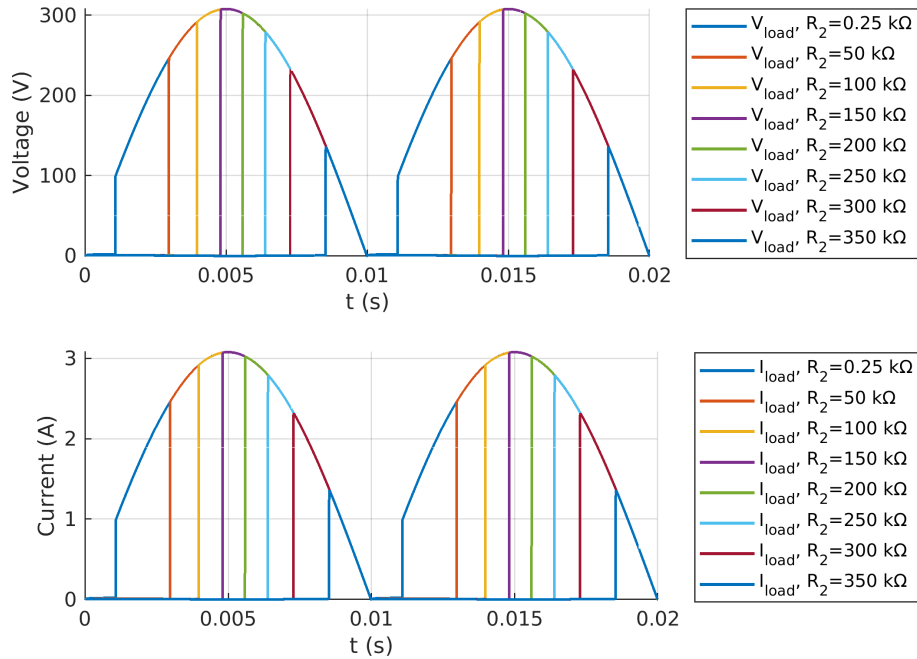

# Simulation Results

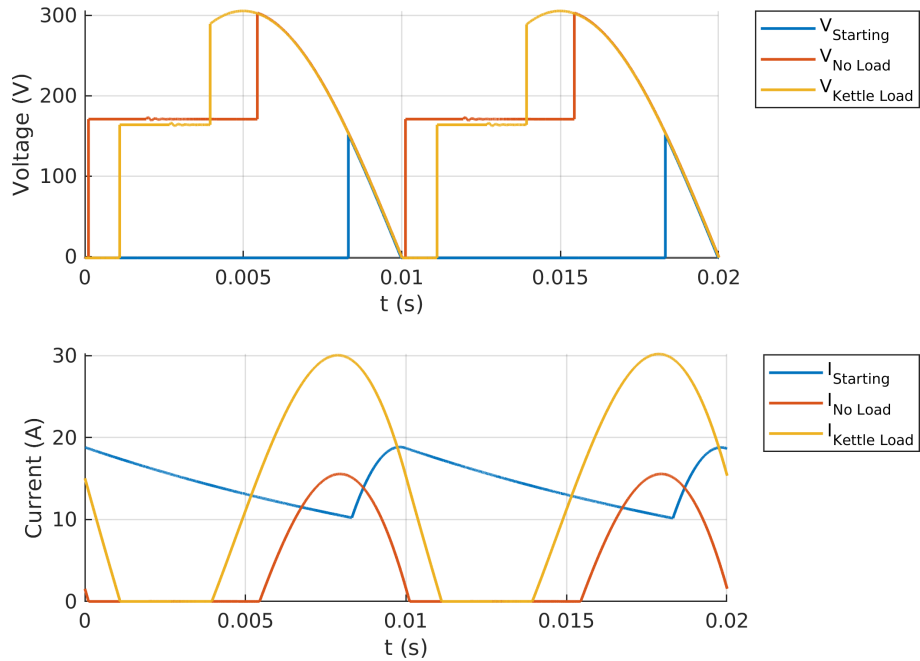

## Key Component Ratings

Maximum component stress from simulation results

- Triac:  $V_{\max} = 311 \text{ V}$ ,  $I_{\text{rms}} = 17.6 \text{ A}$
- Diode Bridge:  $V_{\max} = 306 \text{ V}$ ,  $I_{\text{rms}} = 12.5 \text{ A}$  (per diode)
- Resistors: All  $< 1/4 \text{ W}$ . (But Littlefuse application note recommends  $1/2 \text{ W}$  for  $R_3$ )
- Capacitors:  $< 60 \text{ V}$

## Project Plan

- Complete bill of material
- Procure components ([Direnc.net](#) + Konya Sokak)
- Build prototype
- Test on increasing loads (load bank  $\Rightarrow$  motor)
- Troubleshoot & modify prototype as needed
- Once working prototype is obtained, as time allows
  - Consider modifications for feedback in firing circuit
  - Add remaining touches like enclosure, PCB, etc

## Credit

Nuclear explosion logo made by [Freepik](#) from [Flaticon.com](#)